

MASSACHUSETTS INSTITUTE OF TECHNOLOGY  
Department of Electrical Engineering and Computer Science  
6.301 Solid State Circuits

Fall 2013  
Problem Set 4


Issued : Oct 1, 2013  
Due : Oct 8, 2013

---


**Problem 1: Building Blocks**

The AC schematics for four amplifiers are shown below. For each of the amplifiers, find the midband voltage gain and the -3dB frequency using the open-circuit time-constant method. Assume  $\beta = 200$ ,  $I_C = 2.5\text{mA}$ ,  $c_\pi = 50\text{pF}$ , and  $c_\mu = 2\text{pF}$ . Neglect  $r_b$  and  $r_o$ .


(a) Common Emitter:

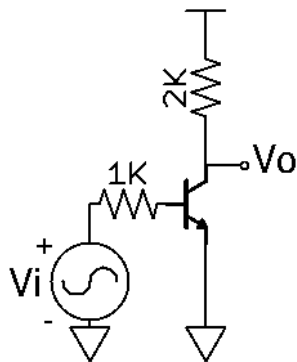


(b) Emitter Follower:

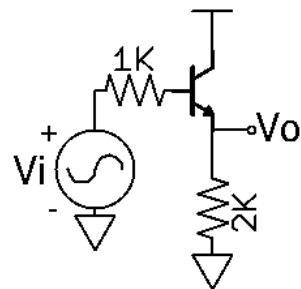

(c) Common Base:

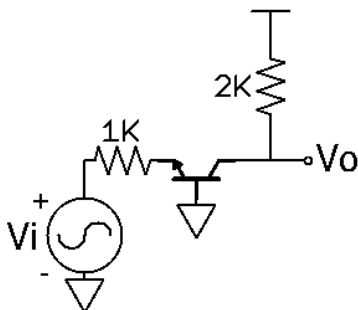


(d) C-E with Emitter Degeneration:

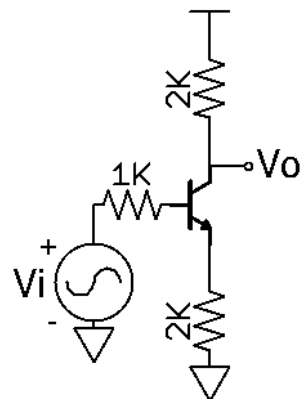
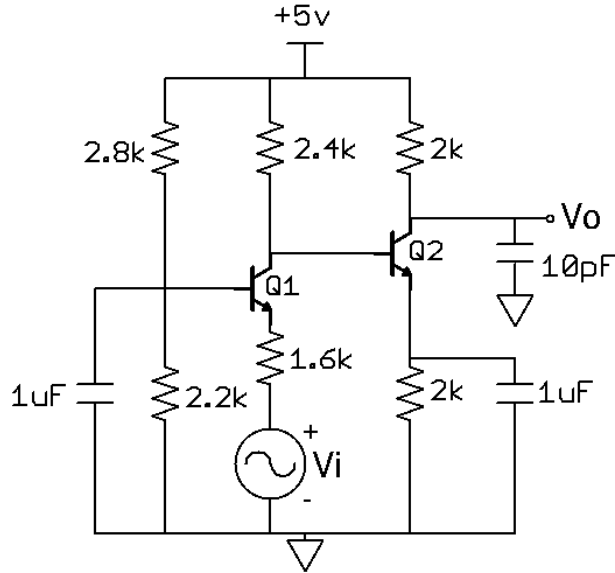
### Problem 2: Two-transistor OCTs

For the following CB-CE amplifier, assume  $V_{BE} = 0.6\text{V}$ ,  $\beta = 200$ ,  $c_{\pi} = 20\text{pF}$ , and  $c_{\mu} = 2\text{pF}$ . Neglect  $r_b$  and  $r_o$ .




- Calculate the midband voltage gain.
- Find the -3dB frequency of the amplifier using the OCT method.

### Problem 3: Emitter Coupled Pairs


For the two amplifiers shown below, find the midband voltage gain and the -3dB frequency. Why does one have more bandwidth than the other?

You may assume  $V_{BE} = 0.6\text{V}$ ,  $\beta = 200$ ,  $c_{\pi} = 40\text{pF}$ ,  $c_{\mu} = 4\text{pF}$ , and neglect  $r_b$  and  $r_o$ .

- Single-ended Differential Pair

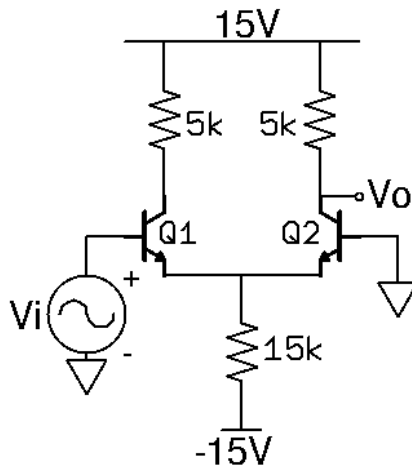


(b) EF-CB

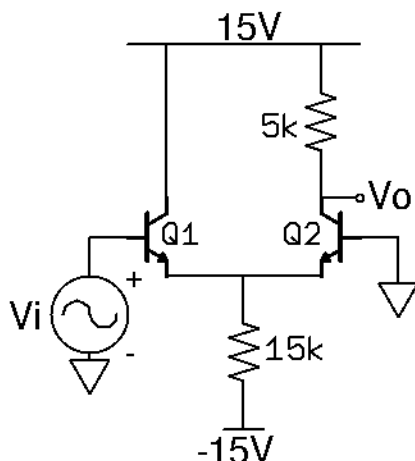
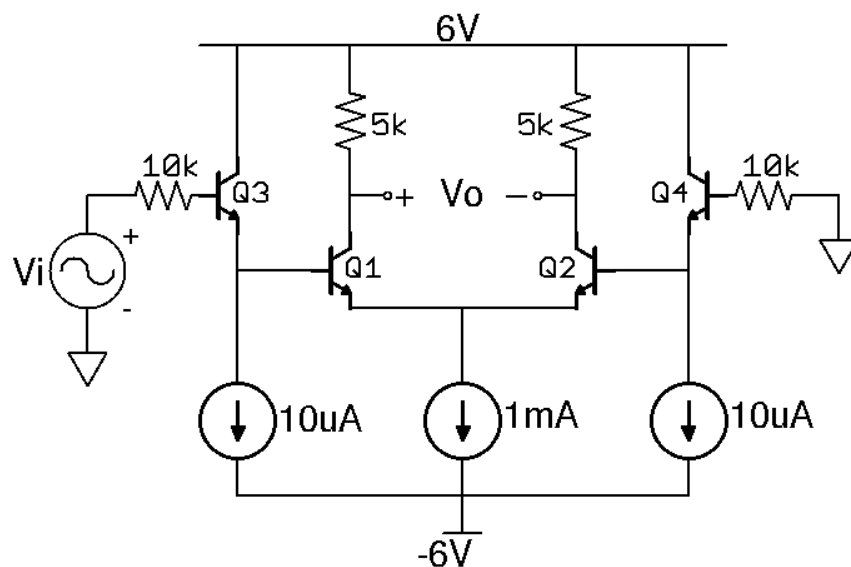
#### Problem 4: Buffered Diff Pair

For the amplifier shown below, use the following data:  $I_s = 0.5\text{fA}$ ,  $\beta = 200$ ,  $c_{\mu 0} = 0.5\text{pF}$ ,  $c_{je} = 4\text{pF}$ , and  $f_T = 500\text{MHz}$  at  $I_C = 1\text{mA}$  and  $V_{CB} = 2.5\text{V}$ .  $m = 0.5$  and  $\Psi_0 = 0.7\text{V}$  for all junctions. Neglect  $r_b$  and  $r_o$ .




- Calculate the midband voltage gain.
- Find the -3dB frequency of the amplifier using the OCT method.
- Verify the above results in SPICE. Turn in your SPICE input file as well as a plot showing the high-frequency roll-off.


### Problem 5: Cascode Cascades

Given the following AC schematics, find the midband gain and -3dB frequency using the OCT method for each amplifier. You may assume  $\beta = 200$ ,  $c_\mu = 2\text{pF}$ ,  $c_{je} = 5\text{pF}$ , and  $\tau_F = 250\text{ps}$ . Neglect  $r_b$  and  $r_o$ .

(a)

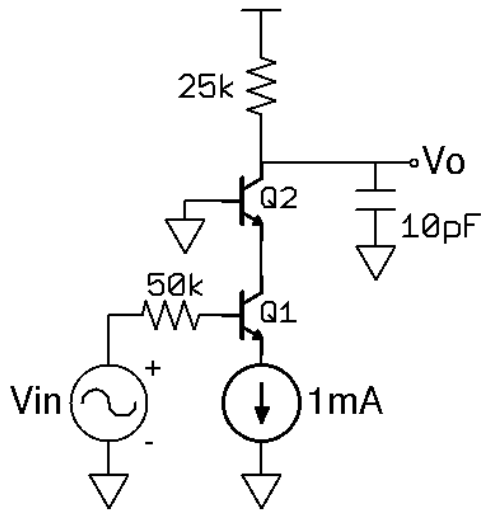

(b)

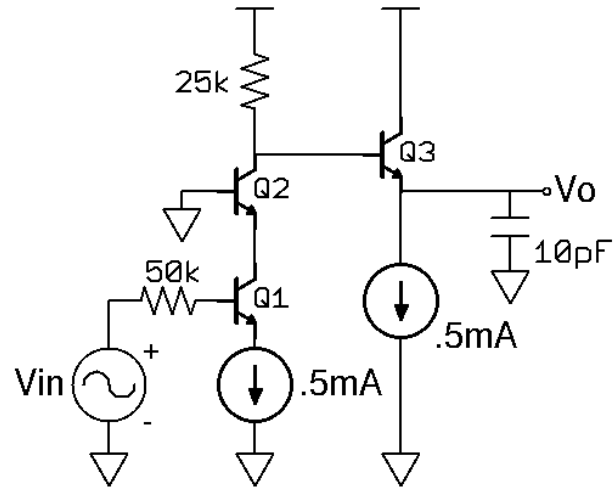

(c)

