

MASSACHUSETTS INSTITUTE OF TECHNOLOGY
Department of Electrical Engineering and Computer Science
6.301 Solid State Circuits

Fall 2013
Problem Set 8





Issued : Nov 19, 2013
Due : Nov 26, 2013



Problem 1: Translinear Jungle Gym

For each of the following circuits use the Gilbert Principle to determine I_o as a function of the other circuit variables. All of these circuits simplify to simple expressions.

A differential output is denoted by an I_o superimposed on an arrow, and double emitter arrows with $2A_E$ indicate that transistor has double the emitter area of the other transistors, thus its I_S is twice as large.

Finally, use the method of open circuit time constants to estimate the $-3dB$ frequency for the circuit in part (a) only.

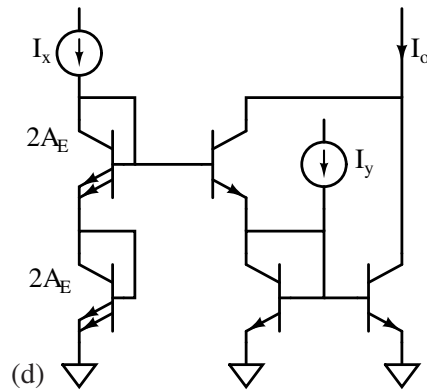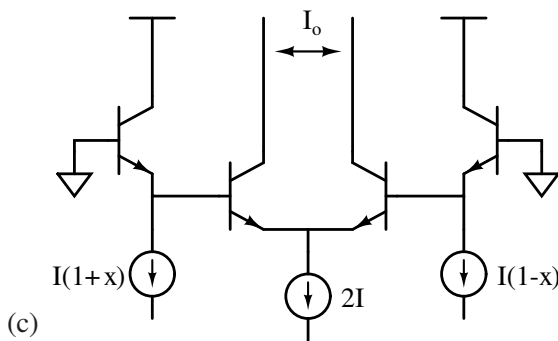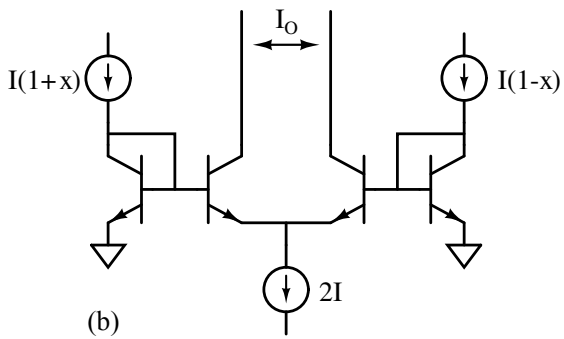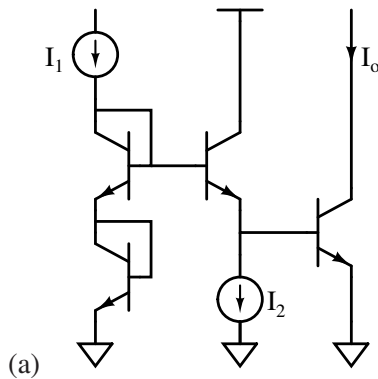


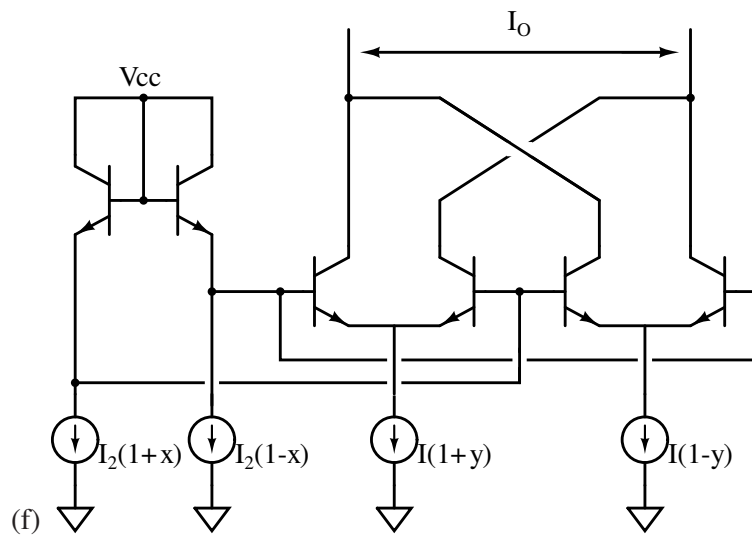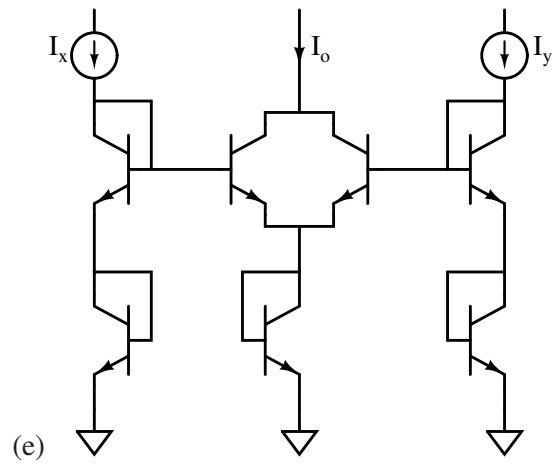

Problem 2: Translinear Approximator


Find $I_o = f(I_x)$, assuming well-matched transistors, negligible base currents, and $I_1 = 1A$. Also assume Q_A and Q_B have emitter areas $24A_E$ and $2A_E$, respectively, while all other transistors have emitter area A_E .

What famous function does I_o approximate for small I_x ?

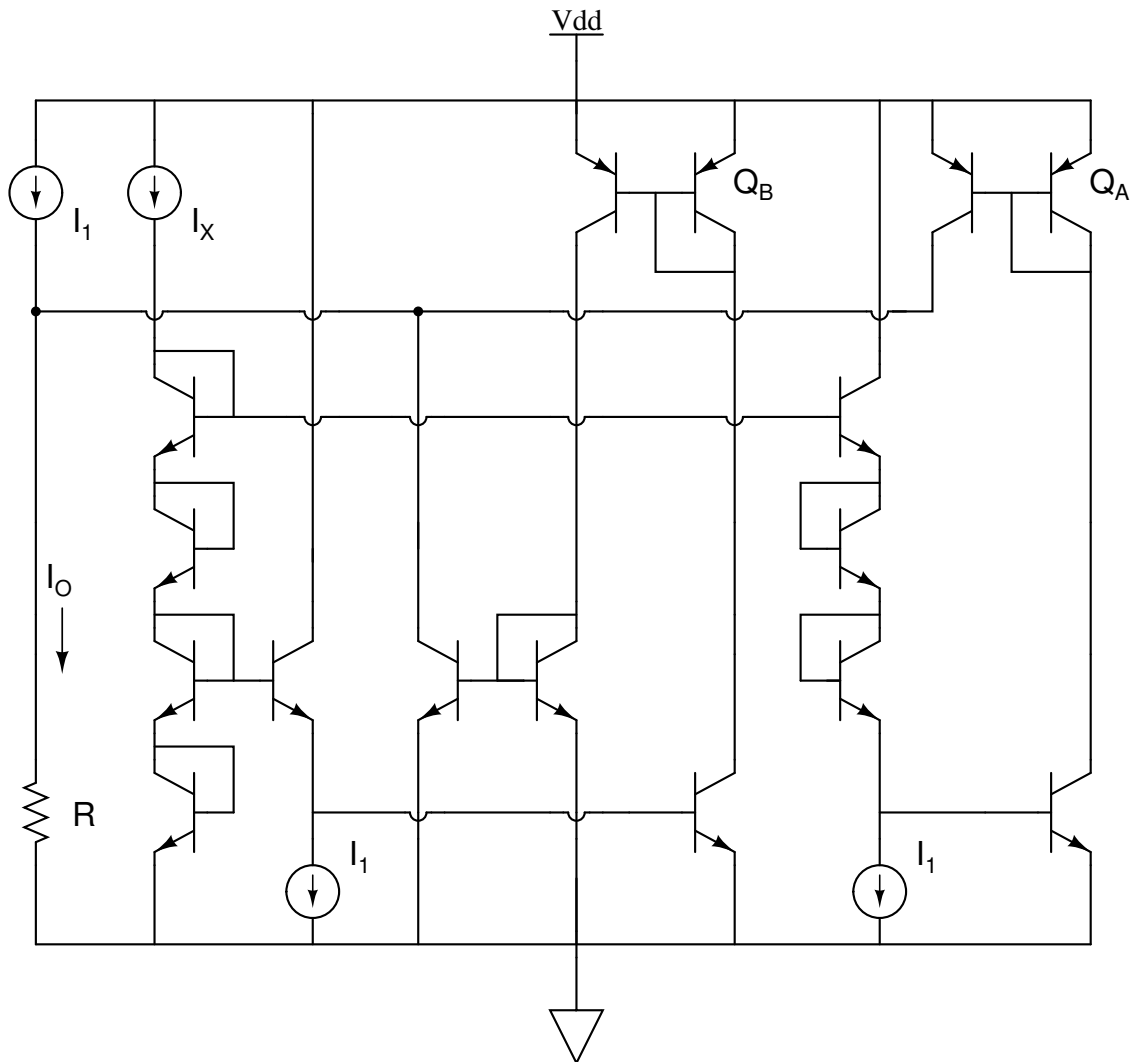

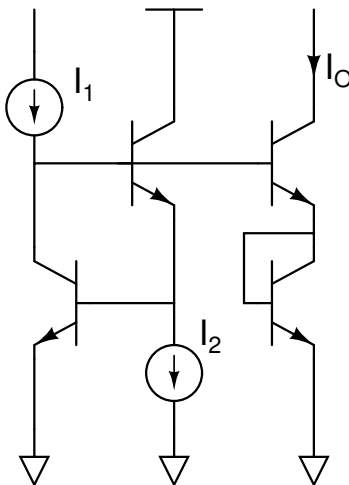Problem 3: Base Current Effects

In the following circuit, assume $I_2 = 1mA$ and $\beta = 100$.



- Express I_o in terms of I_1 and I_2 .
- Assume we can tolerate a maximum I_o error due to β of 50%. For what range of I_1 is this circuit valid?

Problem 4: Temperature Dependence

When we design a circuit, we prefer that it operate over a wide range of temperature. In the following circuit, assume that $\frac{1}{R} \frac{dR}{dT} = 600ppm/^{\circ}C$ and $\frac{dV_{be}}{dT} = -2mV/^{\circ}C$.

For each of the following circuits find $\frac{dI_o}{dT}$.

Additionally, find the value of R_E in terms of I_o that minimizes $\frac{dI_o}{dT}$.

