

MASSACHUSETTS INSTITUTE OF TECHNOLOGY
Department of Electrical Engineering and Computer Science
6.301 Solid State Circuits


Fall 2013
Problem Set 4

Issued : Oct 1, 2013
Due : Oct 8, 2013


Problem 1: Building Blocks

The AC schematics for four amplifiers are shown below. For each of the amplifiers, find the midband voltage gain and the -3dB frequency using the open-circuit time-constant method. Assume $\beta = 200$, $I_C = 2.5\text{mA}$, $c_\pi = 50\text{pF}$, and $c_\mu = 2\text{pF}$. Neglect r_b and r_o .


(a) Common Emitter:

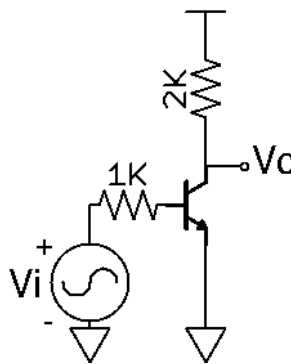


(b) Emitter Follower:

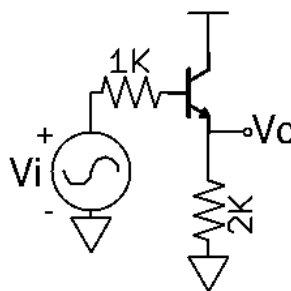

(c) Common Base:

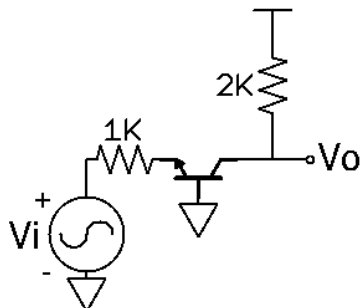

(d) Common Emitter with Emitter Degeneration:

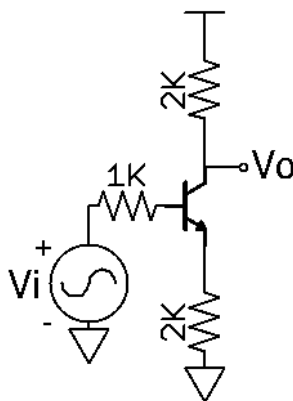

Problem 2: Two-transistor OCTs

For the following CB-CE amplifier, assume $V_{BE} = 0.6v$, $\beta = 200$, $c_\pi = 20pF$, and $c_\mu = 2pF$. Neglect r_b and r_o .

- Calculate the midband voltage gain.
- Find the -3dB frequency of the amplifier using the OCT method.

Problem 3: Emitter Coupled Pairs

For the two amplifiers shown below, find the midband voltage gain and the -3dB frequency. Why does one have more bandwidth than the other?

You may assume $V_{BE} = 0.6v$, $\beta = 400$, $c_\pi = 40pF$, $c_\mu = 4pF$, and neglect r_b and r_o .

- Single-ended Differential Pair
- EF-CB