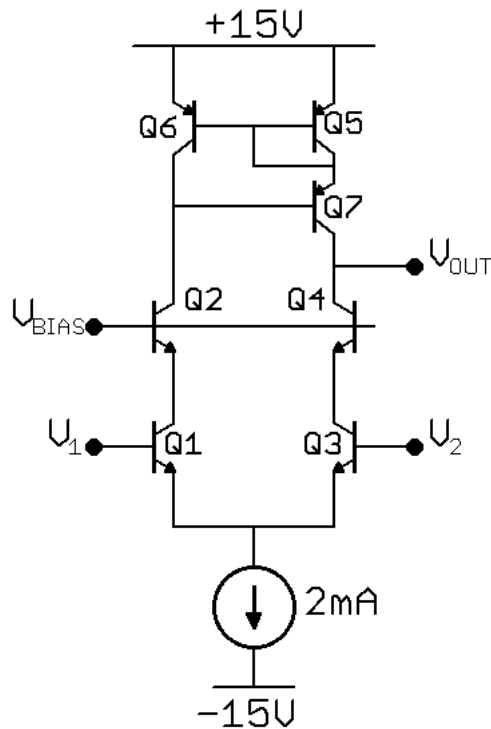


MASSACHUSETTS INSTITUTE OF TECHNOLOGY
Department of Electrical Engineering and Computer Science
6.301 Solid State Circuits

Fall 2013
Problem Set 6

Issued : Oct 22, 2013
Due : Oct 29, 2013


Problem 1: Differential Pair with Active Load



Find $\frac{v_{out}}{v_1 - v_2}$ at midband, assuming $\beta_{nnp} = 200$, $\beta_{pnp} = 50$, $V_{A,npn} = 100V$, $V_{A,pnp} = 50V$, Common-Mode Voltage $V_{CM} = 0$, and $V_{BIAS} = 4V$.

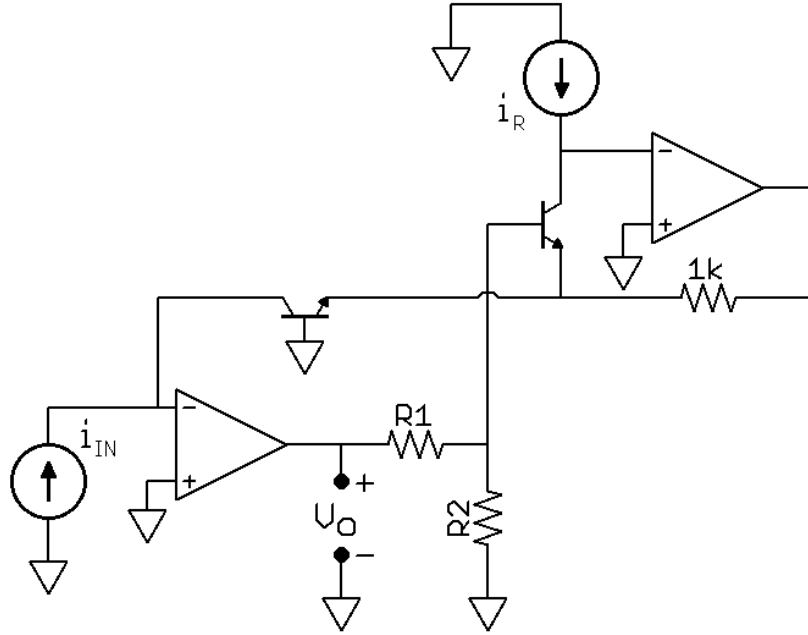Problem 2: Op Amp Applications


Assume the following circuit is operating at room temperature ($T = 300K$)



- When $R_1 = 15.7R_2$, v_o is of the form $v_o = A \log_{10}(x)$. Find A and x .
- Solve for R_1 in terms of R_2 such that $v_o = A \log_2(x)$ behavior.

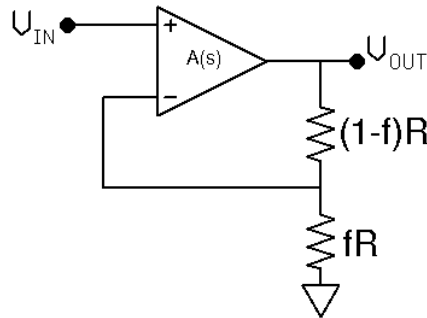
Problem 3: Op Amp Frequency Response

The following op amp has a finite gain with frequency response $A(s) = \frac{a_o}{\tau s + 1}$
 $a_o = 10^6$, $\tau = 10^{-6}$, and $f = [1, 0.1, 0.01, 0.001]$.



- Solve for the closed-loop DC gain and upper -3dB frequency for each value of f .
- Sketch the Bode Plot magnitude of $\frac{V_{OUT}}{V_{IN}}(s)$ for each value of f on one plot.
- What effect does f (gain) have on the step response?

Problem 4: Op Amp Filter

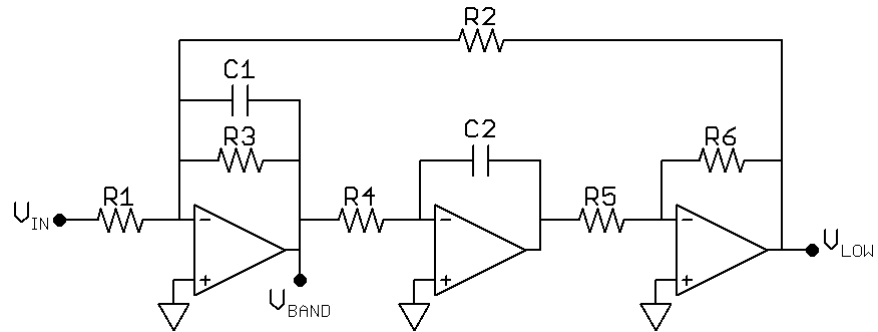

Find the transfer functions $\frac{V_{LOW}}{V_{IN}}(s)$ and $\frac{V_{BAND}}{V_{IN}}(s)$ such that the denominator is of the form:

$$D(s) = s^2 + \zeta\omega_o s + \omega_o^2 \quad (1)$$

Find ζ and ω_o .