

MASSACHUSETTS INSTITUTE OF TECHNOLOGY  
Department of Electrical Engineering and Computer Science  
6.301 Solid State Circuits

Fall 2013  
Problem Set 8





Issued : Nov 19, 2013  
Due : Nov 26, 2013



**Problem 1: Translinear Jungle Gym**

For each of the following circuits use the Gilbert Principle to determine  $I_o$  as a function of the other circuit variables. All of these circuits simplify to simple expressions.

A differential output is denoted by an  $I_o$  superimposed on an arrow, and double emitter arrows with  $2A_E$  indicate that transistor has double the emitter area of the other transistors, thus its  $I_S$  is twice as large.

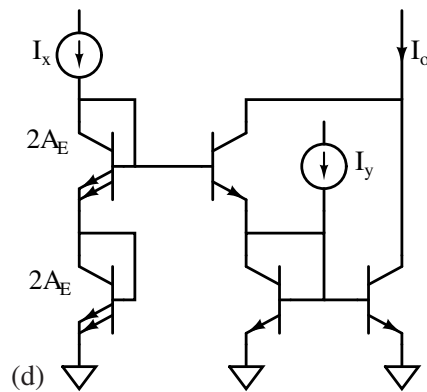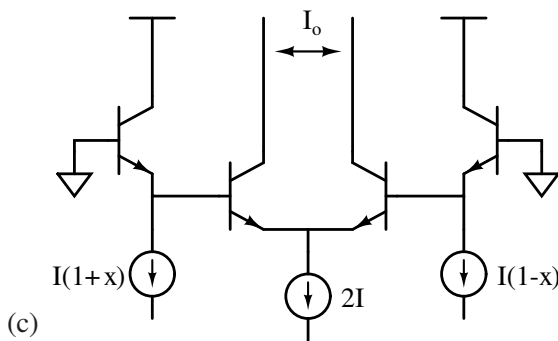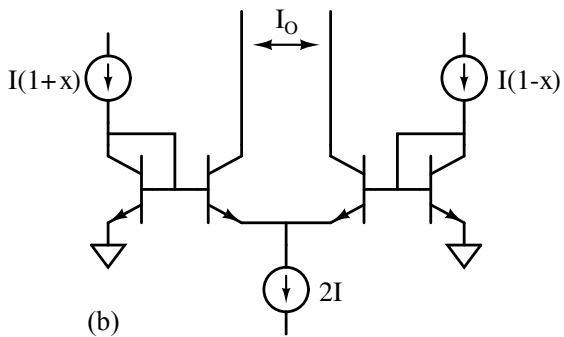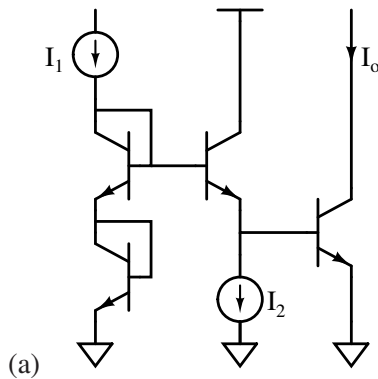Finally, use the method of open circuit time constants to estimate the  $-3dB$  frequency for the circuit in part (a) only.




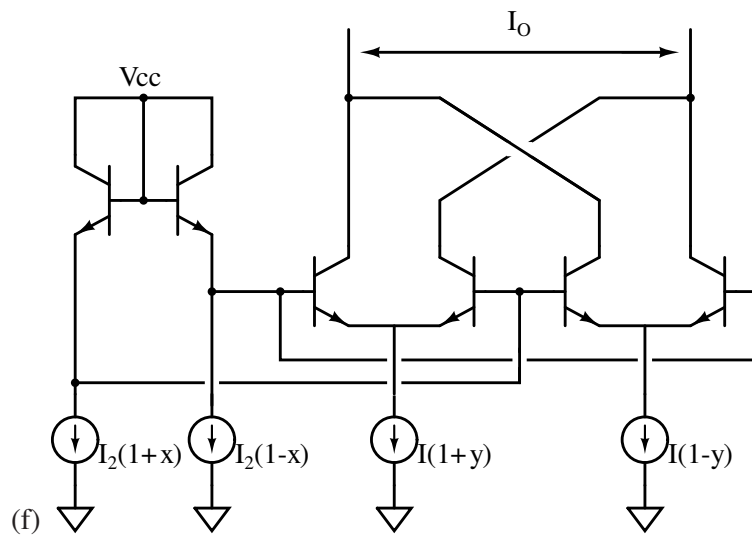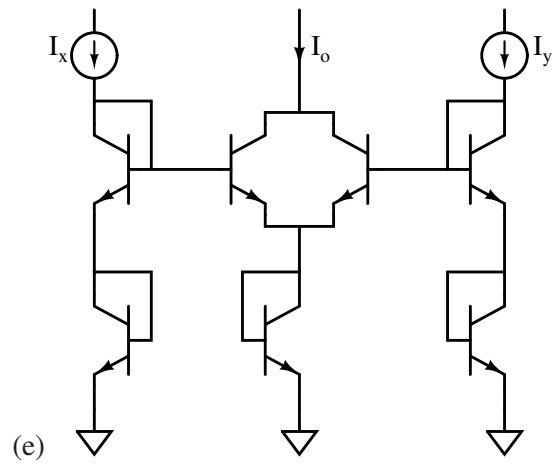
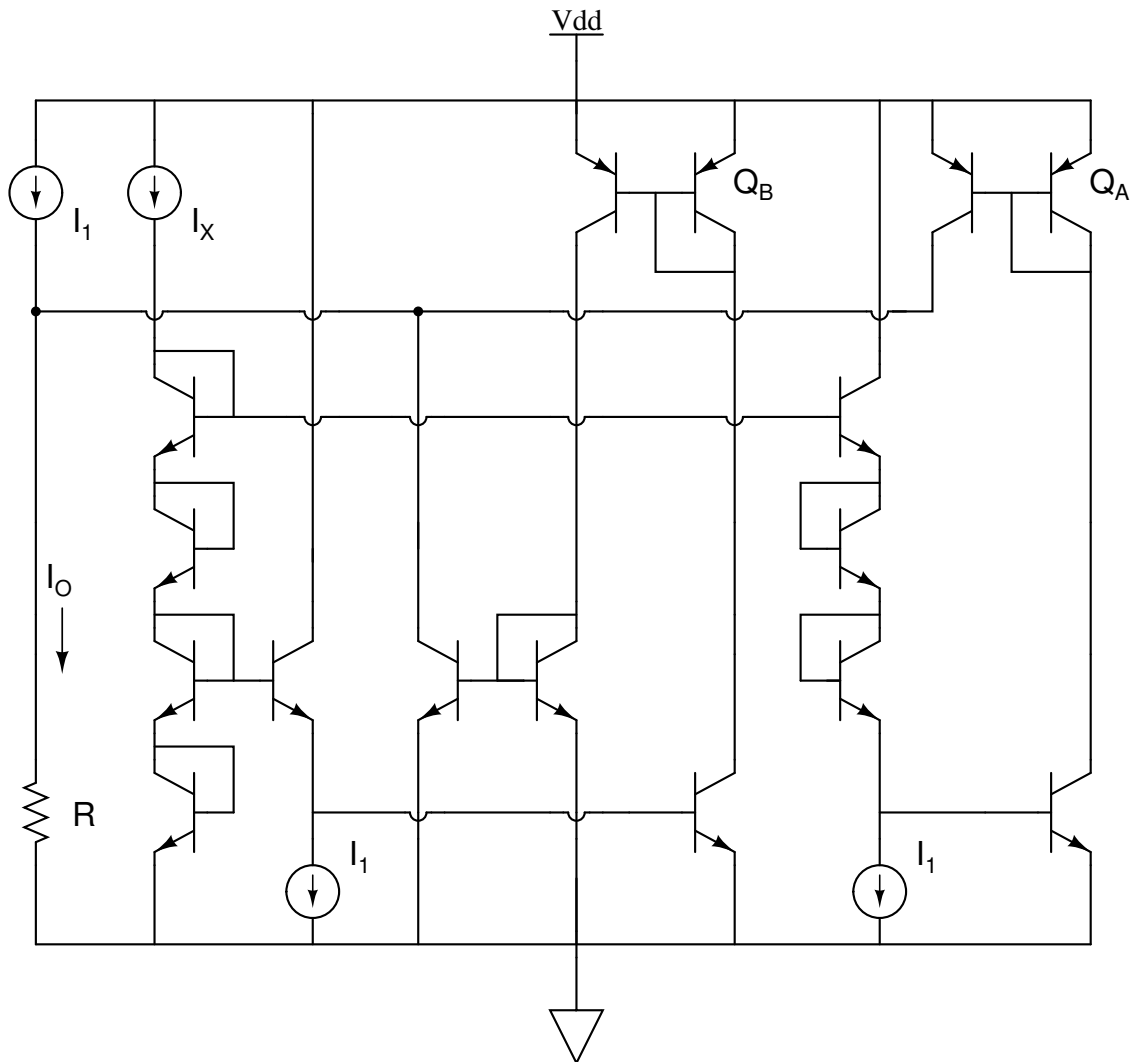
### Problem 2: Translinear Approximator


Find  $I_o = f(I_x)$ , assuming well-matched transistors, negligible base currents, and  $I_1 = 1A$ . Also assume  $Q_A$  and  $Q_B$  have emitter areas  $24A_E$  and  $2A_E$ , respectively, while all other transistors have emitter area  $A_E$ .

What famous function does  $I_o$  approximate for small  $I_x$ ?


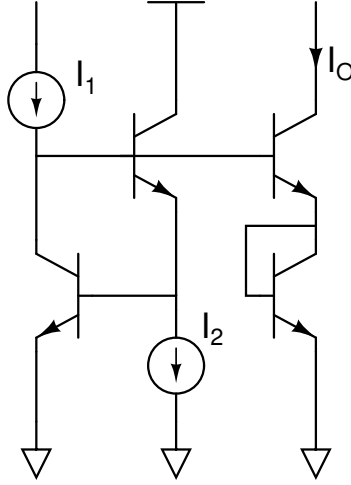
### Problem 3: Base Current Error


In the following circuit, assume  $I_2 = 1mA$  and  $\beta = 100$ .



- Express  $I_o$  in terms of  $I_1$  and  $I_2$ .
- Assume we can tolerate a maximum  $I_o$  error due to  $\beta$  of 50%. For what range of  $I_1$  is this circuit valid?
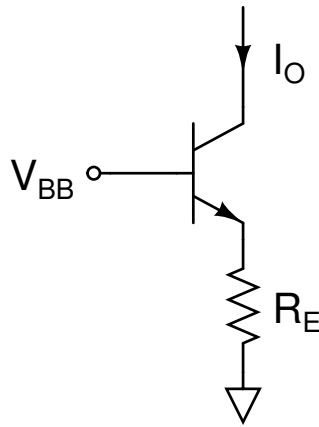
### Problem 4: Temperature Dependence and Compensation

When we design a circuit, we prefer that it operate over a wide range of temperature. Below is a voltage-biased current source with a temperature dependence heavily based on  $R_E$  and  $V_{be}$ . In the following circuit, assume that  $\frac{1}{R} \frac{dR}{dT} = 600ppm/^{\circ}C$  and  $\frac{dV_{be}}{dT} = -2mV/^{\circ}C$ .



- Find  $\frac{dI_o}{dT}$ .
- Find the value of  $R_E$  in terms of  $I_o$  that minimizes  $\frac{dI_o}{dT}$ .

**Problem 5: Your Own Personal Bandgap**

Referencing the simplified schematic of the LM109 5V Bandgap Reference from lecture, design a modified version that produces an output voltage of 7.5V.

Explain the operation of your reference.