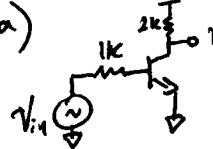

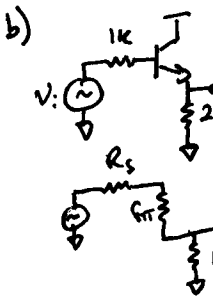


Set 4 solutions


1) $\beta = 200, I_C = 2.5 \text{ mA}, C_\pi = 50 \text{ pF}, C_\mu = 2 \text{ pF} \quad r_b = 0, r_o = \infty \quad \left. \begin{array}{l} \rightarrow g_m = \frac{I_C}{V_T} = 0.1 \text{ V} \\ r_\pi = \frac{\beta}{g_m} = 2 \text{ k} \end{array} \right\}$

a) 
$$a_v = \frac{-r_\pi}{R_s + r_\pi} g_m R_L = -133.3$$



$$\begin{aligned} r_{\pi_0} &= r_\pi \parallel R_s = 666.6 \Omega \rightarrow \tau_{\pi_0} = C_\pi r_{\pi_0} = 33.3 \text{ ns} \\ \tau_{\mu_0} &= r_\pi \parallel R_s + R_L + g_m R_L r_\pi \parallel R_s \approx 136 \text{ k} \rightarrow \tau_{\mu_0} = C_\mu r_{\mu_0} = 272 \text{ ns} \\ f_{-3\text{dB}} &= \frac{1}{2\pi(\tau_{\mu_0} + \tau_{\pi_0})} = 521 \text{ kHz} \end{aligned}$$

b) 
$$a_v = \frac{(\beta+1)R_E}{(\beta+1)R_E + r_\pi + R_s} = 0.993$$
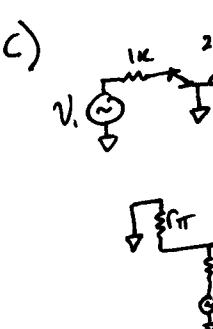
$$\begin{aligned} r_{\pi_0} &= r_\pi \parallel \frac{R_s + R_E}{1 + g_m R_E} = 14.8 \Omega \rightarrow \tau_{\pi_0} = .74 \text{ ns} \\ r_{\mu_0} &= R_s \parallel (r_\pi + (\beta+1)R_E) = 997 \Omega \rightarrow \tau_{\mu_0} = 2 \text{ ns} \\ f_{-3\text{dB}} &= \frac{1}{2\pi \cdot 2.74 \text{ ns}} = 58.1 \text{ MHz} \end{aligned}$$


c) 
$$a_v = \frac{\beta R_L}{(\beta+1)R_s + r_\pi} = 1.97$$

$$\begin{aligned} r_{\pi_0} &= r_\pi \parallel \frac{R_s}{1 + g_m R_s} = 9.9 \Omega \rightarrow \tau_{\pi_0} = .493 \text{ ns} \\ r_{\mu_0} &= R_L = 2 \text{ k} \rightarrow \tau_{\mu_0} = 4 \text{ ns} \\ f_{-3\text{dB}} &= \frac{1}{2\pi \cdot 4.493 \text{ ns}} = 35.4 \text{ MHz} \end{aligned}$$

d) 
$$a_v = \frac{-g_m R_L r_\pi}{r_\pi + R_s + (\beta+1)R_E} = -0.99$$

$$\begin{aligned} r_{\pi_0} &= r_\pi \parallel \left(\frac{R_s + R_E}{1 + g_m R_E} \right) = 14.8 \Omega \rightarrow \tau_{\pi_0} = .74 \text{ ns} \\ r_{\mu_0} &= R_s \parallel (r_\pi + (\beta+1)R_E) + R_L + \left(\frac{g_m r_\pi}{r_\pi + (\beta+1)R_E} \right) (R_s \parallel (r_\pi + (\beta+1)R_E)) R_L = 3985 \Omega \\ \tau_{\mu_0} &= 7.97 \mu\text{s} \\ f_{-3\text{dB}} &= \frac{1}{2\pi(8.71 \text{ ns})} = 18.27 \text{ MHz} \end{aligned}$$

2)

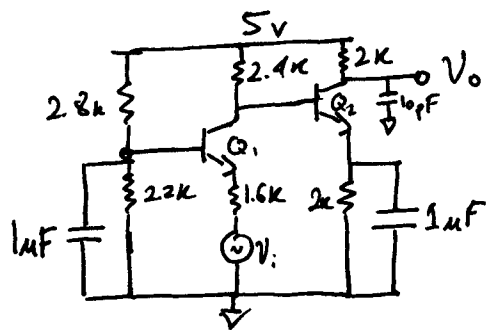

$$V_{BE} = 0.6V \quad \beta = 200 \quad C_{\pi} = 20pF \quad C_{\mu} = 2pF \quad r_b = 0 \quad r_o = \infty$$

a) Midband Voltage gain:

$$V_{B_1} = 2.2V$$

$$V_{E_1} = 2.2V - 0.6V = 1.6V$$

$$I_{C_1} \approx \frac{1.6V}{1.6k} = 1mA \rightarrow g_{m1} = 0.04S, r_{\pi1} = 5k\Omega$$

$$V_{B_2} = 2.6V$$

$$V_{E_2} = 2V$$


$$I_{C_2} = \frac{2V}{2k} = 1mA \rightarrow g_{m2} = 0.04S$$

$$r_{\pi2} = 5k\Omega$$

Stage 1 is a Common base Amplifier. Stage 2 is a Common Emitter amp.

$$a_v = \frac{\beta R_L}{(1+\beta)R_E + r_{\pi}}$$

$$a_v = -g_{m2} R_L$$

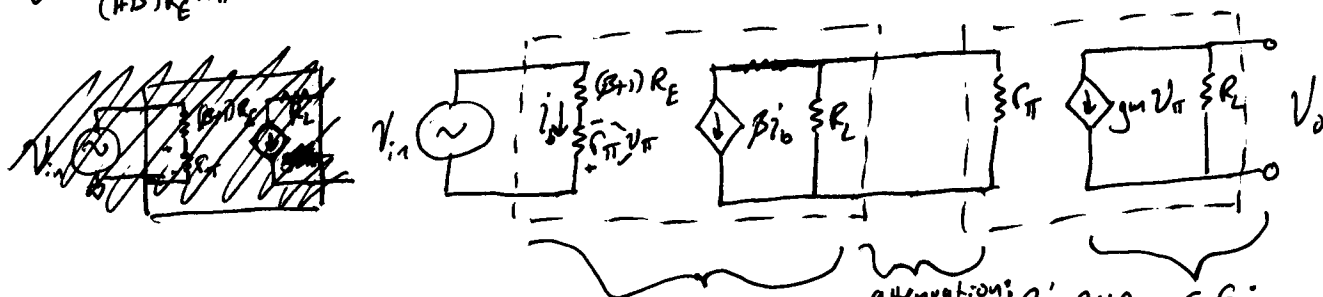

$$CB: a_v = \frac{\beta R_L}{(1+\beta)R_E + r_{\pi}} \approx \frac{R_L}{R_E}$$

attenuation:

$$R_L' = R_L || r_{\pi}$$

CE:

$$a_v = -g_{m2} R_L$$

$$\text{Total gain: } -g_{m2} R_L \times \frac{\beta(R_L || r_{\pi})}{(1+\beta)R_E + r_{\pi}} = -79.4$$

b)

$$r_{\pi01} = r_{\pi1} || \frac{R_{E1}}{1+g_{m1}R_{E1}} = 24.5\Omega$$

$$r_{\mu01} = R_{L1} || r_{\pi2} = 1.62k\Omega$$

$$\tau_{\pi1} = .49ns$$

$$\tau_{\mu1} = 3.24ns$$

$$r_{\pi02} = r_{\pi2} || R_{L1} = 1.62k\Omega$$

$$r_{\mu02} = r_{\pi2} || R_{L1} + R_{L2} + g_{m2}R_{L2}(r_{\pi2} || R_{L1}) = 133.22k\Omega$$


$$\tau_{\pi2} = 32.4ns \quad \tau_{os} = (10pF)(2k\Omega) = 20ns$$

$$\tau_{\mu2} = 266.44ns$$

$$\sum \tau = 322.57ns \rightarrow f_{3dB} = 494kHz$$

3) Find $a_v + f_{-3dB}$ for both amplifiers below
 $V_{BE} = 0.6V$, $\beta = 200$, $C_{\pi} = 40pF$, $C_{\mu} = 4pF$, $R_b = 0$, $R_o = \infty$

a)

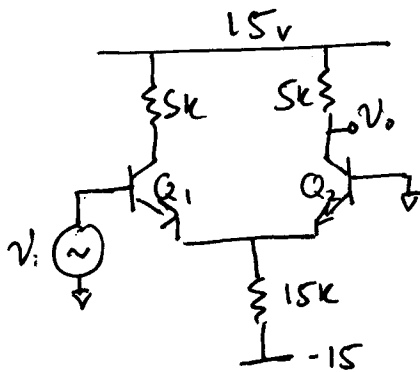

$$V_E = 0 - 0.6V \rightarrow I_{RE} = \frac{14.4V}{15k\Omega} = .96mA$$


Current in both $Q_1 + Q_2$ are the same:

$$I_{C1} = I_{C2} = 0.48mA$$

Differential Gain: Half-circuit analysis:

$$V_{in,diff} = V_1 - V_2 = V_i$$

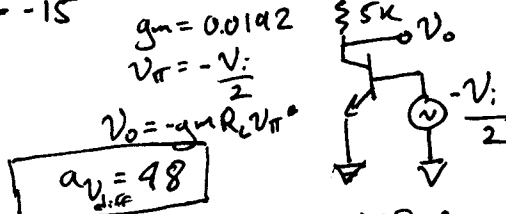We can model this single-ended input as a differential input with half the amplitude.




$$g_m = 0.0192$$

$$v_{\pi} = -\frac{V_i}{2}$$

$$v_o = -g_m R_{L\pi} v_{\pi}$$

$$a_{v,diff} = 48$$

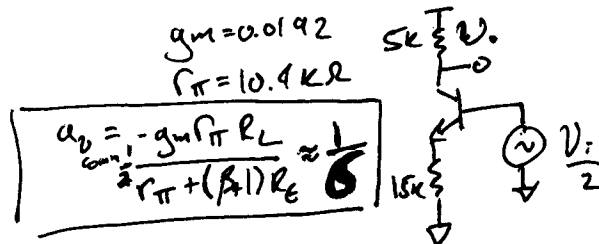Common Mode Gain: Half-circuit analysis: $V_{in,common} = \frac{V_1 + V_2}{2} = \frac{V_i}{2}$



$$g_m = 0.0192$$

$$r_{\pi} = 10.4k\Omega$$

$$a_{v,common} = \frac{-g_m r_{\pi} R_L}{r_{\pi} + (\beta + 1) R_E} \approx \frac{1}{6}$$

There is also a common-mode component to this input. we'll see if it makes a difference.
 → Doesn't!

OCT'S:

$$r_E = \frac{r_{\pi}}{\beta + 1} \parallel R_E = 9.5\Omega$$


$$r_{\pi o1} = r_{\pi} \parallel \frac{R_S + r_E}{1 + g_m r_E} = 25.8\Omega \rightarrow \tau_{\pi o1} = 1.03ns$$

$$\tau_{M o1} = R_L C_{\mu} = 20ns$$

$$r_{\pi o2} = r_{\pi} \parallel \frac{r_E}{1 + g_m r_E} = 25.8\Omega \rightarrow \tau_{\pi o2} = 1.03ns$$


$$\tau_{M o2} = R_L C_{\mu} = 20ns$$
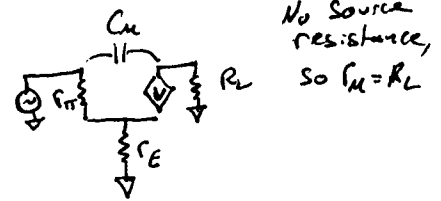
$$\Sigma = 42.06ns \rightarrow f_{-3dB} = 3.78MHz$$



No source resistance, so $r_{\mu} = R_L$

5)

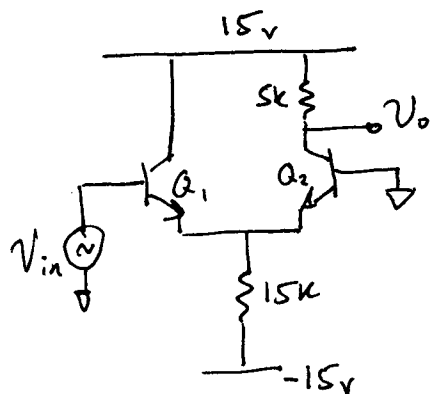

All bias parameters are identical.
Half-circuit analysis is identical. You could analyze it by thinking about an EF-CB cascade.
Answer is the same.

$$a_{v,d.f} = 48$$

$$a_{v,common} \approx \frac{1}{6}$$

OCT'S:


Same $\rightarrow r_{\pi 01} = r_{\pi} \parallel \frac{r_E}{1 + g_m r_E} = 25.8 \Omega \rightarrow \tau_{\pi 01} = \tau_{\pi 02} = 1.03 \text{ ns}$

Same $\rightarrow r_{m02} = R_L = 5 \text{ k}\Omega \rightarrow \tau_{m02} = 20 \text{ ns}$

$r_{m01} = 0 \rightarrow \tau_{m01} = 0 \text{ ns}$

$$\tau' = 22.06 \text{ ns}$$

$$f_{-3dB} = 7.22 \text{ MHz}$$

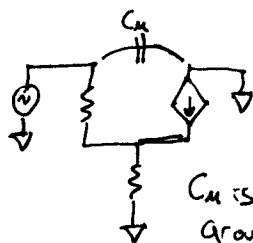


C_u is incrementally grounded on both ends $\rightarrow r_{m01} = 0$

According to OCT'S, this amplifier will operate twice as fast as the previous amplifier, due to incrementally grounding the collector of Q_1 .

* In Practice:

Since we are using Q_1 to steer current in Q_2 , it turns out that we don't care about the voltage gain in Q_1 . While the voltage gain is attenuated in Q_1 at $f_{-3dB_1} = 3.78 \text{ MHz}$, the current gain goes unaffected (C_u begins to source i_c). Thus τ_{m01} should actually be ignored when calculating the ~~OCT'S~~ -3dB bandwidth.

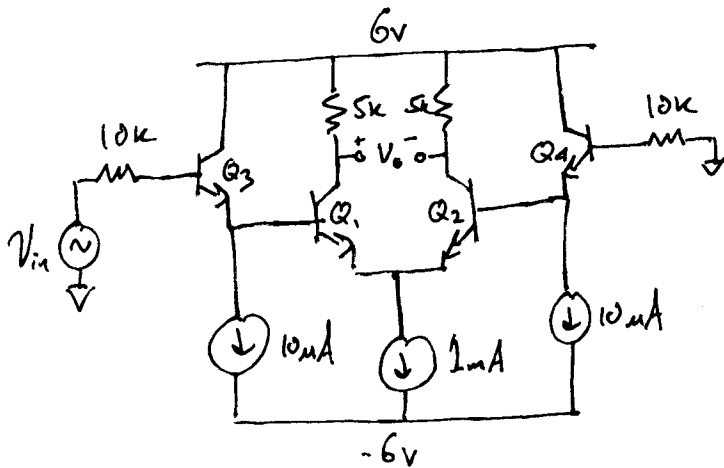
4) $I_S = 0.5 \text{ fA}$ $\beta = 200$ $C_{u0} = 0.5 \text{ pF}$ $C_{je} = 4 \text{ pF}$ $f_T = 500 \text{ MHz}$ @ $I_C = 1 \text{ mA}$
 $V_{CB} = 2.5 \text{ V}$
 $m = 0.5 + \Psi_0 = 0.7$ $r_b = 0$ $r_o = \infty$



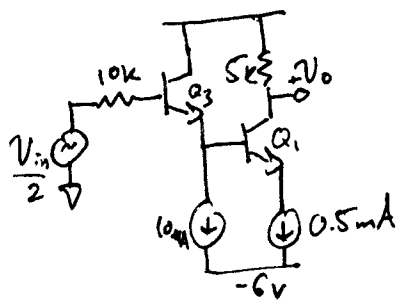a) midband gain:

Common mode: Since the 1mA current source is ideal, the common mode gain ($\approx \frac{R_L}{R_E}$, $R_E \rightarrow \infty$) is zero.

Differential mode: Half-circuit analysis $\rightarrow V_{diff} = V_1 - V_2 = V_{in}$



$$a_{V_{Q3}} = \frac{(\beta+1)R_E}{(\beta+1)R_E + r_{\pi} + R_S} ; R_E \rightarrow \infty \rightarrow a_{V_{Q3}} = 1$$

$$a_{V_{Q1}} = -\frac{r_{\pi}}{R_S + r_{\pi}} g_m R_{L/2} ; R_{S1} = \frac{R_{S3} + r_{\pi}}{\beta+1} = 2.5 \text{ k} \rightarrow a_{V_{Q1}} = -\frac{80}{2}$$

$$a_{V_{diff}} = 2 \times a_{V_{Q1}} = -80$$

b) @ $I_C = 1 \text{ mA}$, $f_T = 500 \text{ MHz} = \frac{g_m}{(C_{\pi} + C_u) 2\pi} \rightarrow C_{\pi} = \frac{g_m}{(2\pi) 500 \text{ MHz}} - C_u$

@ $V_{CB} = 2.5 \text{ V}$ $C_u = \frac{C_{u0}}{(1 + \frac{V_{CB}}{\Psi_c})^m} = \frac{0.5 \text{ pF}}{(1 + \frac{2.5}{0.7})^{0.5}} = 234 \text{ fF}$

$$C_{\pi} = \frac{0.04}{1000\pi \times 10^6} - 234 \text{ fF} = 12.5 \text{ fF}$$

\rightarrow Find τ_F for simulation: $\tau_F = \frac{C_{\pi} - C_{jeF}}{g_m} = \frac{12.5 \text{ fF} - C_{je} \times 2}{0.04} = \frac{12.5 \text{ fF} - 2 \times 4 \text{ fF}}{0.04} = 112.5 \text{ pS} = \tau_F$ for later.

Continued...

b)

$$\text{for } Q_3 + Q_4, \quad V_{BE} = V_T \ln\left(\frac{10 \mu A}{0.53 A}\right) = 0.593 \approx 0.6 V$$

$$V_{CB} = 6 V \rightarrow C_M = \frac{0.5 pF}{\sqrt{1 + \frac{6 V}{0.7 V}}} = 161.6 fF$$

$$C_{\pi} = g_m \tau_F + C_{je} = 8.045 pF$$

$$r_{\pi 3} = r_{\pi 3} \parallel \frac{10 k + r_{\pi 1}}{1 + g_{m3} r_{\pi 1}} = 4 k\Omega \rightarrow \tau_{\pi 3} = 32.2 ns = \tau_{\pi 01} = 32.2 ns$$

$$r_{\mu 3} = r_{\pi 1} \parallel \frac{r_{\pi 3}}{\beta + 1} = 1991 \Omega \rightarrow \tau_{\mu 3} =$$

$$= r_{\pi 1} \parallel \frac{r_{\pi 3}}{\beta + 1} + R_c + g_m R_c r_{\pi 1} \parallel \frac{r_{\pi 3}}{\beta + 1} = 206.1 k\Omega \rightarrow \tau_{\mu 3} =$$

$$= 10 k\Omega \parallel (r_{\pi 3} + (\beta + 1) r_{\pi 1})$$

$$= 10 k\Omega \parallel (r_{\pi 3} + (\beta + 1) r_{\pi 1}) = 9960 \rightarrow \tau_{\mu 3} = \tau_{\mu 01} = 1.61 ns$$

for $Q_1 + Q_2$,

$$V_{CB} = 4.1 V \rightarrow C_M = 140.9 fF$$

$$C_{\pi} = 10.25 pF$$

$$R_S = \frac{10 k + r_{\pi 3}}{\beta + 1} = 2.5 k$$


$$R_c = 5 k$$

$$r_{\pi 01} = r_{\pi 1} \parallel R_S = 2 k \rightarrow \tau_{\pi 01,2} = 20.5 ns \quad R_E = 0$$

$$r_{\mu 01} = r_{\pi 1} \parallel R_S + R_c + g_m R_c r_{\pi 1} \parallel R_S = 207 k \rightarrow \tau_{\mu 01,2} = 39.98 ns$$

$$\Sigma = 188.7 ns \rightarrow f_{-3dB} = 843.5 kHz$$

5)

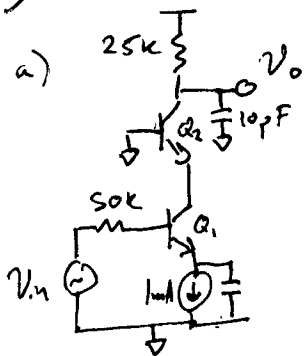

$$\beta = 200, C_M = 2pF, C_{je} = 5pF, \tau_F = 250ps$$

$$C_{\pi} = C_b + C_{jef}; C_b = g_m \tau_F \rightarrow \frac{C_b}{I_c} = \frac{g_m \tau_F}{I_c} = \frac{q}{kT} \tau_F = \frac{10pF}{mA}$$

$$C_{\pi} = 10pF + C_{je} \times 2 = 20pF \quad r_{\pi} = 5k \quad g_m = 0.04$$

$$r_E = \frac{r_{\pi}}{\beta + 1} = 25\Omega$$

$$a_v = \frac{-\beta}{\beta + 1} \left(\frac{r_{\pi} g_m R_L}{R_S + r_{\pi}} \right) = -90$$

$$\tau_{\pi_1} = C_{\pi_1} (R_S \parallel r_{\pi_1}) = 90ns$$

$$\tau_{M_1} = C_{M_1} (R_S \parallel r_{\pi_1} + r_E + g_m r_E R_S \parallel r_{\pi_1}) = 18.2ns$$

$$\tau_{\pi_2} = C_{\pi_2} \left(\frac{r_{\pi}}{\beta + 1} \right) = 0.5ns$$

$$\tau_{M_2} = C_M R_L = 50ns$$


$$\tau_{L_0} = C_M R_L = 250ns$$

$$\sum = 408.7ns$$

$$f_{-3dB} = 389.6kHz$$

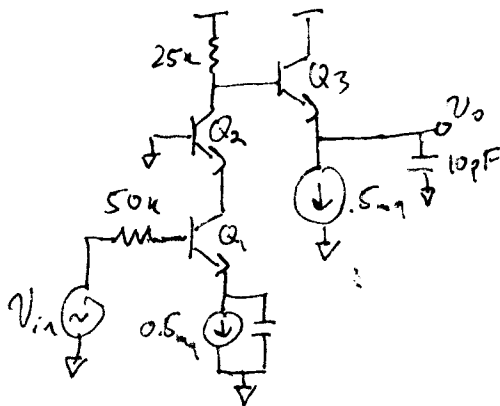b) $C_{\pi} = 5pF + 10pF = 15pF$ $r_{\pi} = 10k$ $g_m = 0.02$ $r_E = \frac{10k}{200} = 50$

$a_{v_3} = 1$, since current source $R_E = \infty$. $r_{inEF} \sim \infty$



$$a_v = \frac{-\beta}{\beta + 1} \left(\frac{r_{\pi} g_m R_L}{R_S + r_{\pi}} \right) = -82.9$$

$$\tau_{\pi_1} = 125ns$$

$$\tau_{M_1} = 33.4ns$$

$$\tau_{\pi_2} = 0.74ns$$

$$\tau_{M_2} = 50ns$$

$$\tau_{\pi_3} = \frac{C_{\pi}}{g_m} = 0.75ns$$

$$\tau_{M_3} = C_M R_L = 50ns$$

$$\tau_{L_0} = C_L \left(\frac{R_L + r_{\pi}}{\beta + 1} \right) = 1.78ns$$

Same ↑

$$\sum = 261ns$$


$$f_{-3dB} = 608.7kHz$$

c)

$$I_C = \frac{1}{3} \mu A \rightarrow g_m = 0.013 \rightarrow r_{\pi} = 15000 \text{ } \Omega$$

$$C_{\pi} = 13.33 \text{ pF}$$

$$r_E = \frac{15 \mu}{200} = 75 \Omega$$

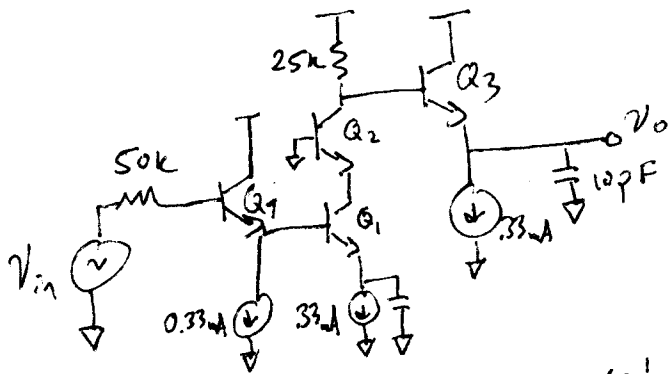

$$a_v = - \frac{(\beta+1) r_{\pi} g_m R_L}{R_S + r_{\pi} + (\beta+1) r_E} = 318$$

$$R_S' = \frac{R_S + r_{\pi}}{\beta+1} \leftarrow \text{Source resistance into Cascode.}$$

$$= 323.4 \Omega$$

$$\tau_{\pi_1} = C_{\pi} (R_S' \parallel r_{\pi}) = 4.2 \text{ ns}$$

$$\tau_{M_1} = C_u (R_S' \parallel r_{\pi} + r_E + g_m r_E R_S' \parallel r_{\pi}) = 1.4 \text{ ns}$$

$$\tau_{\pi_2} = C_{\pi} \left(\frac{r_{\pi}}{\beta+1} \right) = 0.99 \text{ ns}$$

$$\tau_{M_2} = C_u R_L = 50 \text{ ns}$$

$$\tau_{\pi_3} = \frac{C_{\pi}}{g_m} = 1 \text{ ns}$$

$$\tau_{M_3} = C_u R_L = 50 \text{ ns}$$

$$\tau_{\pi_4} = C_{\pi} \left(\frac{R_S + r_{\pi}}{\beta+1} \right) = 4.3 \text{ ns}$$

$$\tau_{M_4} = C_u R_S = 100 \text{ ns}$$

$$\tau_{L_0} = C_L \left(\frac{R_L + r_{\pi}}{\beta+1} \right) = 1.99 \text{ ns}$$

$$\sum = 213.89$$

$$f_{-3dB} = 744.4 \text{ kHz}$$